

**Objective:** This material is part of a disciplinary sequence designed to cover the fundamental concepts of Basic Electrical Engineering.


**Outcomes:** Learn the basic principles and properties of Basic Electrical Engineering

**Level:** Basic


**Prerequisite:** Basic Calculus, Trigonometry & Algebra
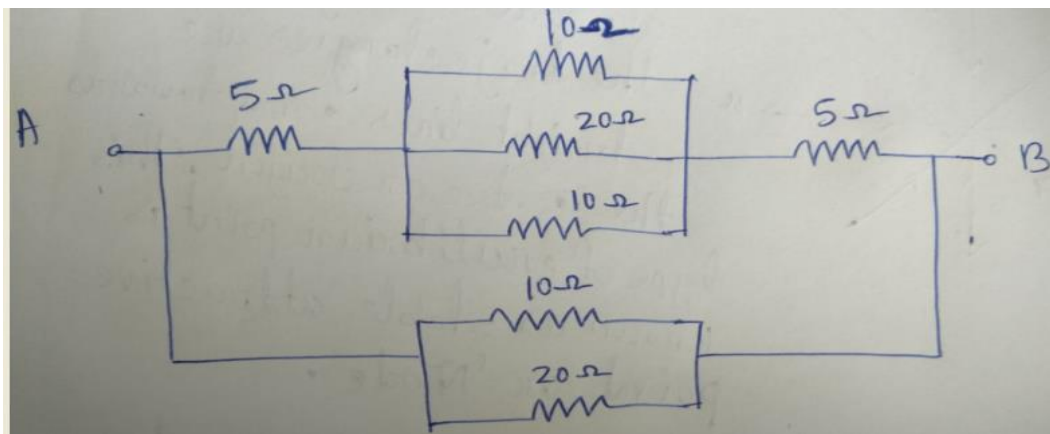
## Assignment-1

- Find the equivalent resistance between points A and B.




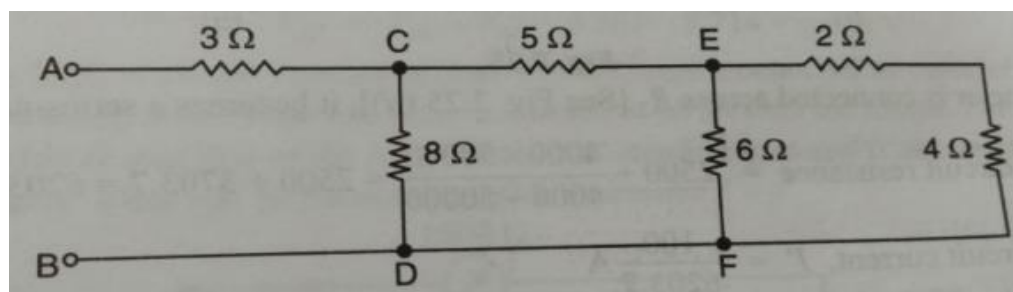- Find the equivalent resistance of the following circuits.




i.


ii.

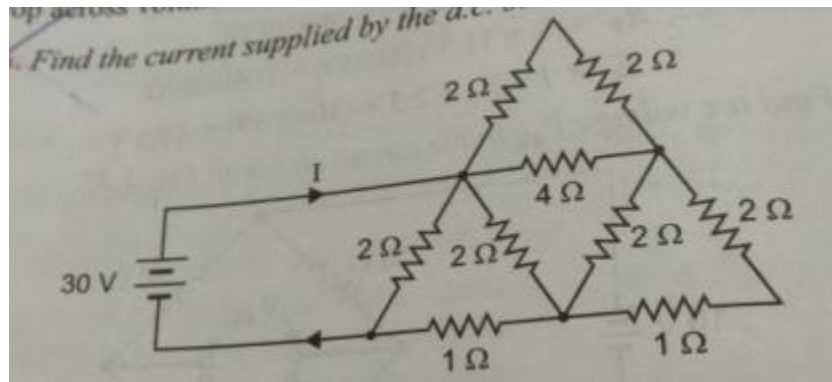


iii.

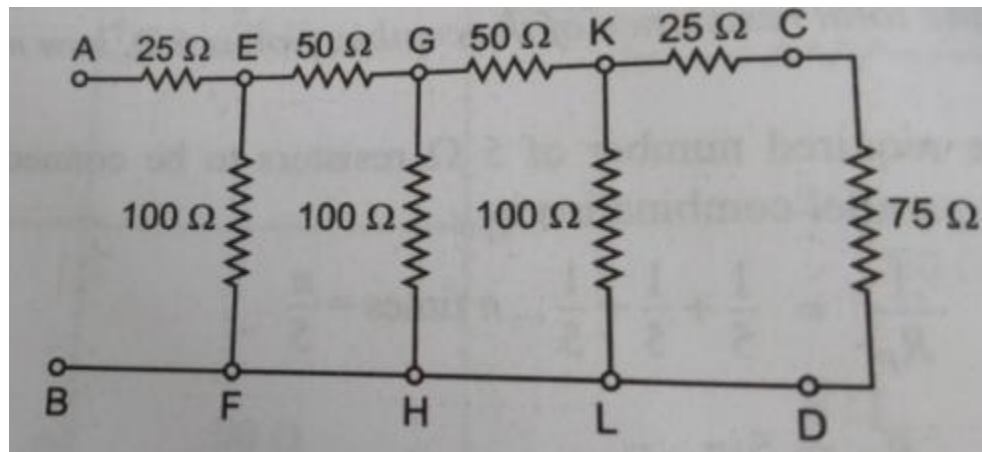

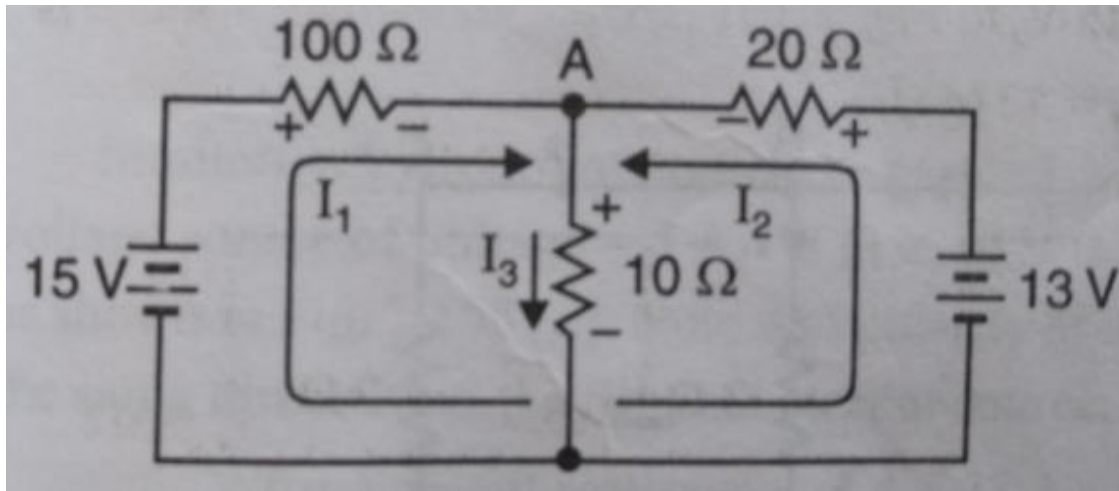
3. Find the current in various resistors in the circuit shown in fig below, by converting voltage sources into current sources.



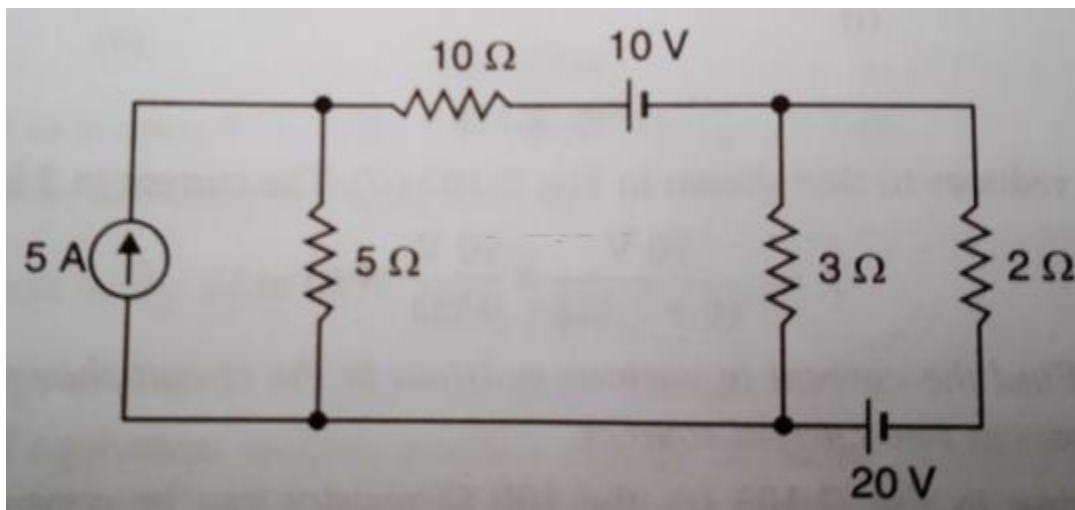
4. Find the current in and voltage across  $2\Omega$  resistor.



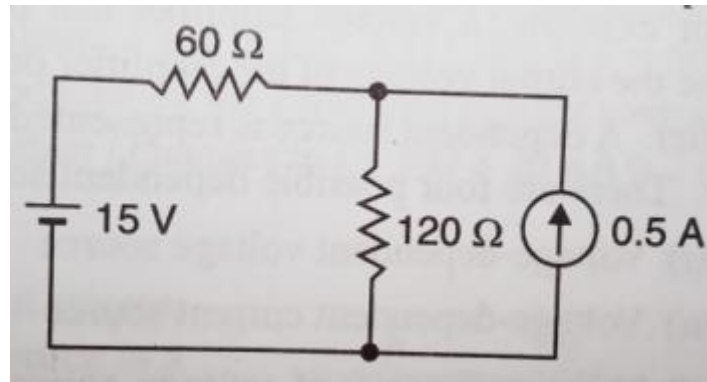5. By performing an appropriate source conversion, find the voltage across  $120\Omega$  resistor in the circuit shown in fig below.



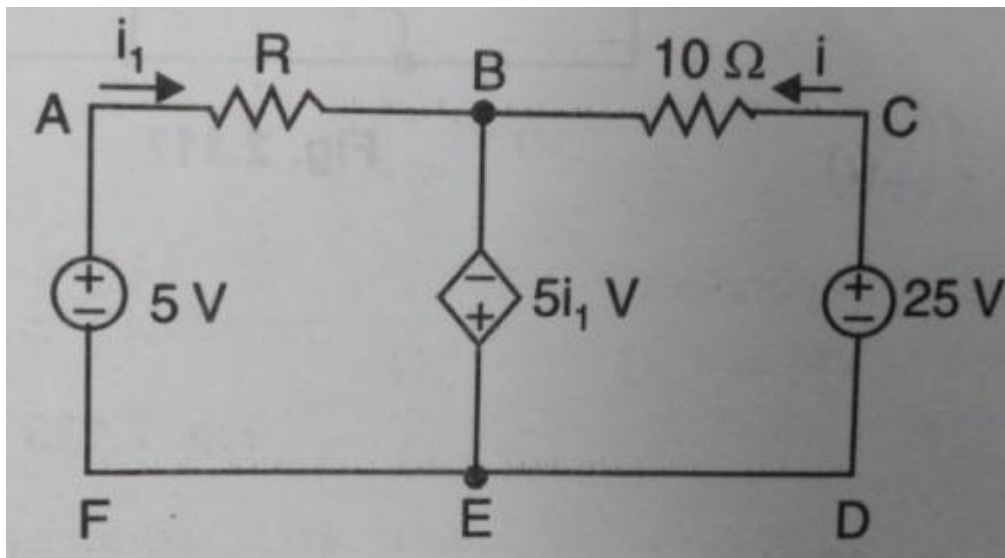6. Find the value of  $i$  in the circuit shown in fig below, if  $R = 10\Omega$ .



7. Find the values of current  $i$  and voltage drops  $v_1$  and  $v_2$  in the circuit of fig below, which contains a current-dependent voltage source. What is the voltage of the dependent-source? All resistance values are in ohms.

